



Poorman's ALU: Milestone 5

Project Iteration 2 Release

04.30.2023

Ryan Woodward

Grand Canyon University
SWE450 - Embedded Systems 2
Prof. Mark Reha



GRAND CANYON
UNIVERSITY™



Table of Contents

Design Specification Report	2
General Technical Approach	3
System Design	4
Application Design	4
Digital Logic Design	5
4-bit Adder/Subtractor (Arithmetic Unit)	5
Quad 2:1 Multiplexer	8
Boolean Logic Unit	10
BCD Decoder	11
PoormansALU	13
PoormansALU Project	15
VLSI Design	17
4-bit Adder/Subtractor (Arithmetic Unit)	17
Quad 2:1 Multiplexer	20
Boolean Logic Unit	22
BCD Decoder	25
BCD Decoder (extended)	26
PoormansALU	27
PoormansALU Project	29
Risks & Issues	30
Other Documentation	31
Resources	33

Design Specification Report


Topic	Milestone 4: Project Iteration Release 3		
Date	April 30, 2023		
Revision	4.0		
Milestone Summary			
	User Story/Task	Hours Worked	Hours Remaining
	Code Refinement	2+	0
	Arm Assembly Code	4+	1+
	IP Core Addition	2+	0
Github URL	Ryanjwoodward/Poormans_ALU: Dedicated Repository for my SWE450 (Embedded Systems 2) Poormans ALU Project (github.com)		
Screencast URL	https://youtu.be/qGbF3a6-ZJk		




General Technical Approach

As this is the final release of the project there was initially little more than tasks of refining the project such as adding further comments to the code and setting up another repository that was clean and navigable. However, after activity 7 I wanted to add more to the project namely an IP block and some Arm assembly to the C-file. Those tasks are complete and integrated with the project. This includes testing the project as a whole with these new portions integrated. Furthermore, as a part of the final release of this project I completed the project using Verilog as well and tested that out on the board to ensure that the project worked in both RTLs

System Design

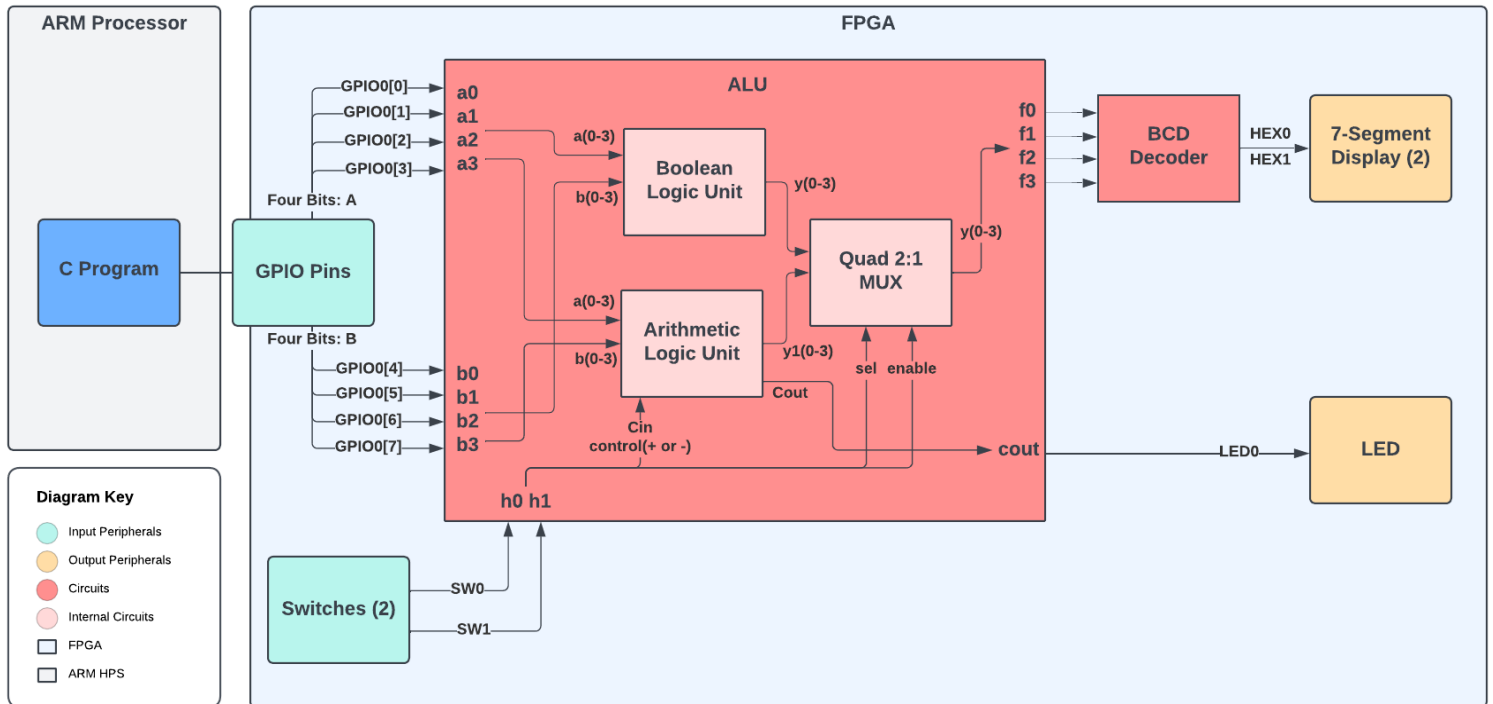

Application Design

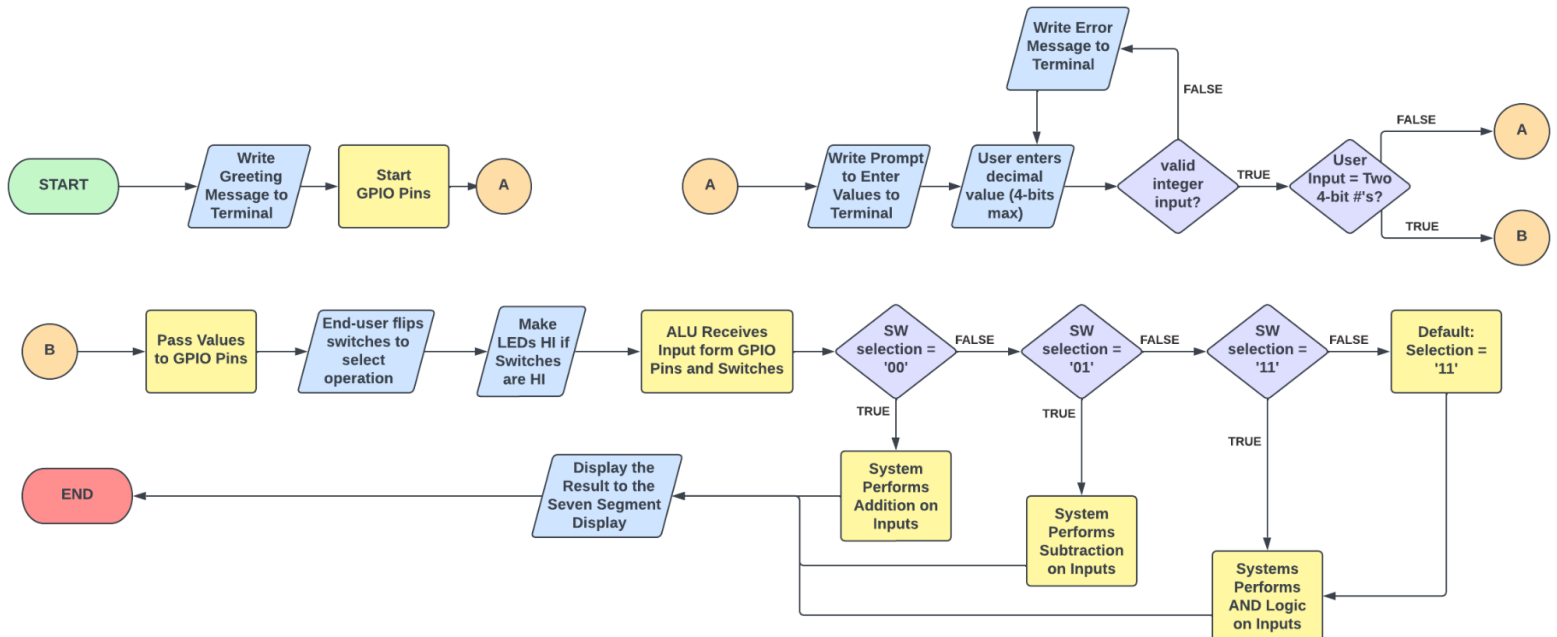

Digital Logic Design


Note: Karnaugh Maps are most suitable for 2-5 variables each of the following circuits is comprised of smaller variants of the circuit (i.e Quad 2:1 MUX to a 2:1 MUX and 4-bit adder/subtractor to 1-bit adder/subtractor) as such I create K-maps and boolean expressions for the smaller circuits making up each of the larger ones. This is because the principle expression and function of each larger circuit can still be demonstrated.

4-bit Adder/Subtractor (Arithmetic Unit)

Arithmetic Unit Truth Table

a3	a2	a1	a0	b3	b2	b1	b0	cin	cout	s3	s2	s1	s0
Cin = '0' (Addition)													
1	0	0	0	1	0	0	0	0	1	0	0	0	0
0	1	0	0	0	1	0	0	0	0	1	0	0	0
1	0	1	0	1	0	1	0	0	1	0	1	0	0
0	1	1	0	0	1	1	0	0	0	1	1	0	0
1	1	1	0	1	1	1	0	0	1	1	1	0	0
0	1	0	1	0	1	0	1	0	0	1	0	1	0
1	1	0	1	1	1	0	1	0	1	1	0	1	0
0	1	1	1	0	1	1	1	0	0	1	1	1	0
1	1	1	1	1	1	1	1	0	1	1	1	1	0
Cin = '1' (Subtraction)													
1	0	0	0	0	1	1	0	1	1	0	0	1	0
0	1	0	0	0	0	1	0	1	1	0	0	1	0
1	1	0	0	1	0	0	0	1	1	0	1	0	0
1	0	0	1	0	1	1	1	1	1	0	0	1	0
1	1	1	0	1	0	1	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1	1	0	1	1	1	1
1	0	0	0	0	1	1	1	1	1	0	0	0	1
1	1	0	1	1	0	0	1	1	1	0	1	0	0
1	1	1	1	1	1	1	1	1	1	0	0	0	0

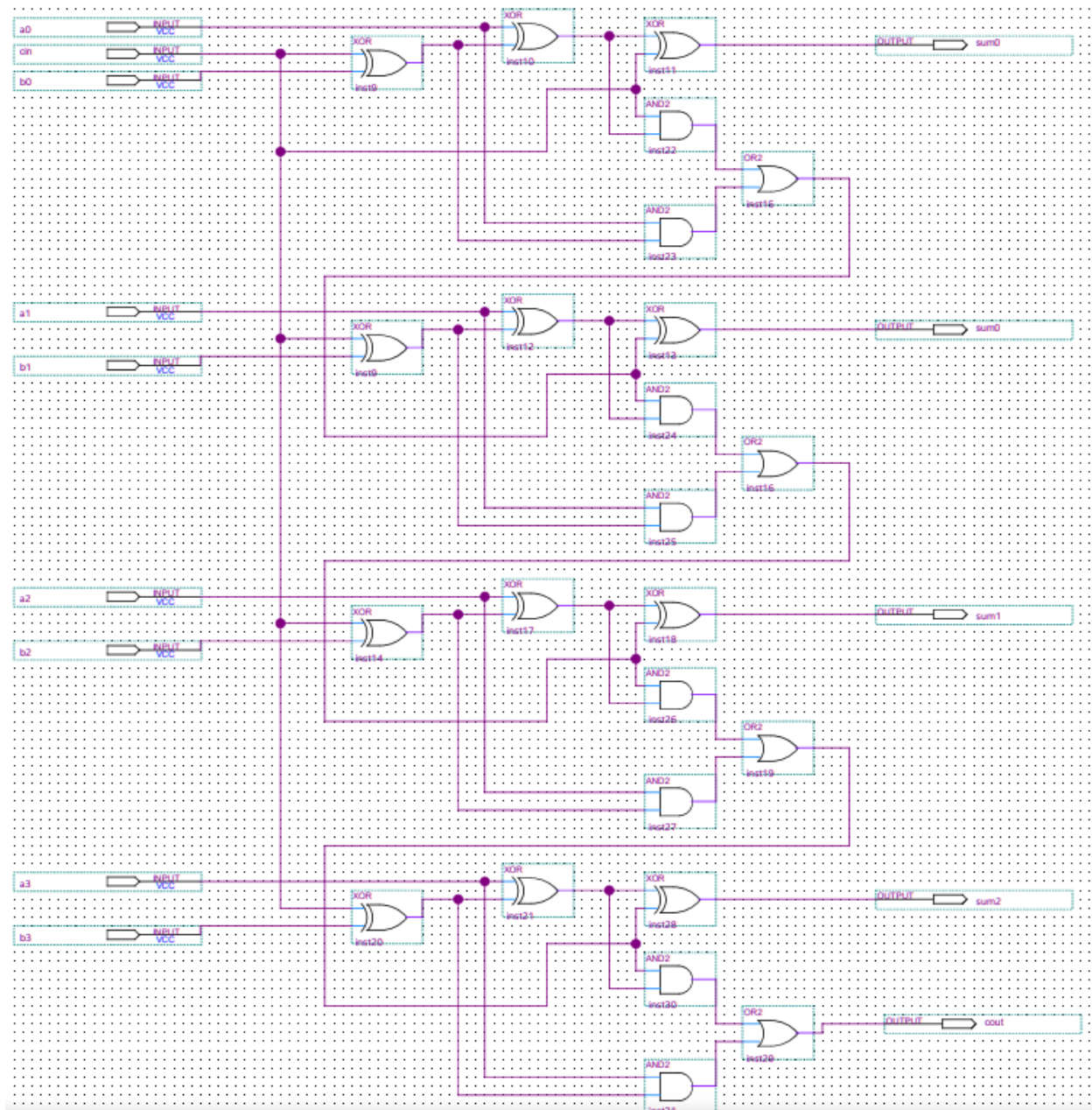4-bit Adder/Subtractor (Arithmetic Unit) Schematic Capture



4-bit Adder/Subtractor Karnaugh Maps

		Sum/Difference						Cout						Bout			
		B, Cin						B, Cin						B, Cin			
A		00	01	11	10	A		00	01	11	10	A		00	01	11	10
0		0	1	0	1	0		0	0	1	0	0		0	1	1	1
1		1	0	1	0	1		0	1	1	1	1		0	0	1	0

Explanation:

The K-map on the left serves to represent the output variables Sum or Difference in a 1-bit adder or subtractor. The middle map represents the Carry out value from a 1-bit adder and the right map represents the Borrow out from a 1-bit subtractor. The difference is the Cin bit is used as a selector to either operation. Extending these maps to a 4-bit wide A and B is simple. Similar to how if A=1 and B=0 the output of Sum is 1 we might see in 4-bits A=1000, B=0000 the result is 1000. Were we to do this for Cout the result would be 0 in both cases because there is no carry. However, for the Bout Table the result is 1 when A=1 and B=0 due to the subtraction operation.

Boolean Expressions

Sum/Difference K-Map

$$S/D = A'B'Cin + AB'Cin' + ABCin + A'BCin'$$

Carry Out K-Map

$$Cout = AB'Cin + ABCin + ABCin' + A'BCin$$

Borrow Out K-Map


$$Bout = A'B'Cin + A'BCin + ABCin + ABCin'$$

Quad 2:1 Multiplexer

Quad 2:1 MUX Truth Table

a3	a2	a1	a0	b3	b2	b1	b0	S	E	f3	f2	f1	f0
1	1	0	1	0	1	0	1	0	0	1	1	0	1
1	1	0	1	0	1	0	1	1	0	0	1	0	1
0	1	1	1	1	0	1	1	0	0	0	1	1	1
0	1	1	1	1	0	1	1	1	0	1	0	1	1
1	1	0	1	0	1	0	1	0	1	0	0	0	0
1	1	0	1	0	1	0	1	1	1	0	0	0	0
0	1	1	1	1	0	1	1	0	1	0	0	0	0
0	1	1	1	1	0	1	1	1	1	0	0	0	0

Quad 2:1 MUX Schematic Capture

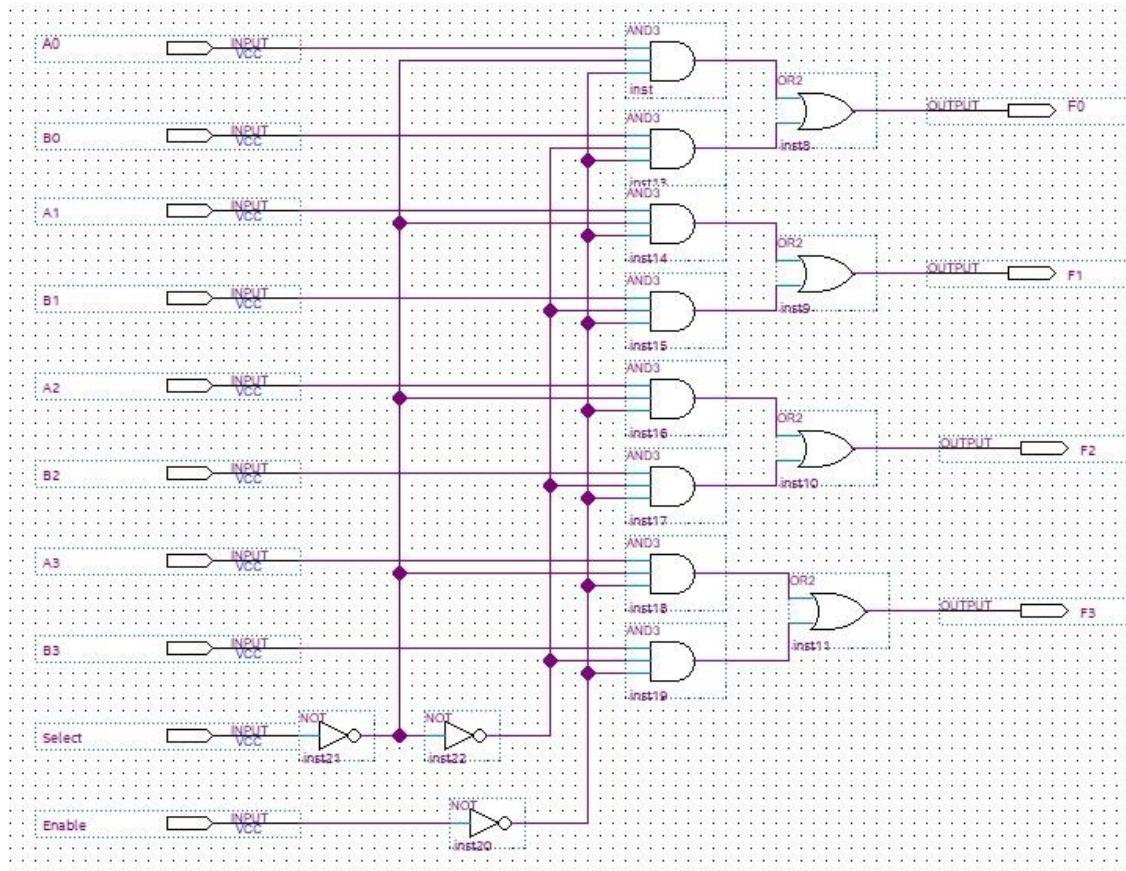

Karnaugh Maps

2:1 MUX

Sel

A, B

	00	01	11	10
0	0	1	1	0
1	0	0	1	1

Explanation

For a 2:1 MUX the output is determined entirely by the Select input, essentially acting as an If-then logic block. If Select is '1' then the output will be A and if Select is Low the output will be B. In my Quad 2:1 MUX this is reversed (Sel =1 Output = B) and there is an additional input of the enable switch when high makes the output 0 regardless of the other inputs. If we include an 'enable' input the K-map looks like:

2:1 MUX w/ Enable

Sel, Enb		A,B			
		00	01	11	10
00		0	1	1	0
01		0	0	0	0
11		0	0	0	0
10		0	0	1	1

Boolean Expression

2:1 MUX

$$F = \text{Sel}'A'B + \text{Sel}'AB + \text{Sel}AB + \text{Sel}AB'$$

Reduce this to: $F = \text{Sel}'B + \text{Sel}A$

2:1 MUX with Enable


$$F = \text{Sel}'B.\text{Enb}' + \text{Sel}A.\text{Enb}'$$

Boolean Logic Unit


Boolean Logic Unit Truth Table

a3	a2	a1	a0	b3	b2	b1	b0	f3	f2	f1	f0
0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0	0	1	0	0
1	0	0	0	1	0	0	0	1	0	0	0
1	1	0	0	1	1	0	0	1	1	0	0
1	0	1	0	0	1	0	1	0	0	0	0
1	0	1	0	1	0	1	0	1	0	1	0
1	1	1	1	1	1	1	1	1	1	1	1
1	1	1	1	0	0	0	0	0	0	0	0
0	0	0	0	1	1	1	1	0	0	0	0

Boolean Logic Unit Schematic Capture

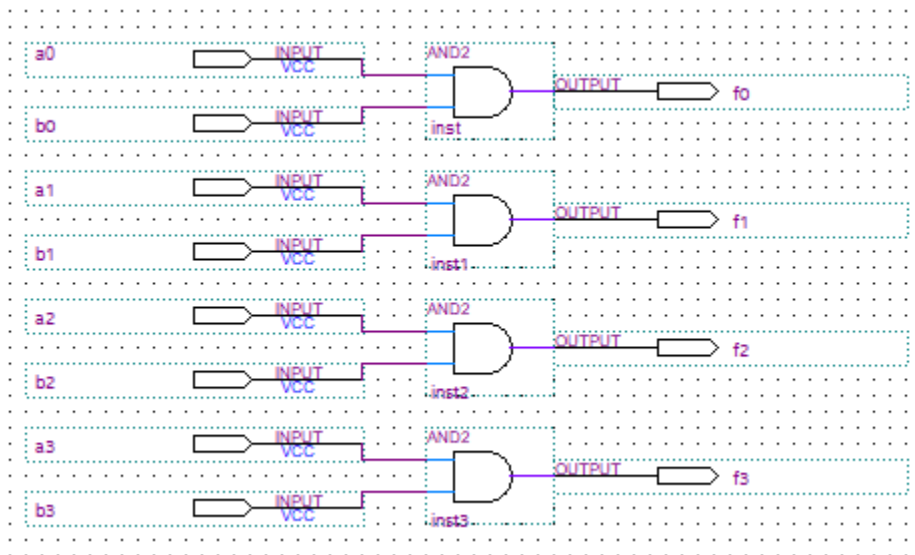

Karnaugh Map

 

Explanation:

Admittedly this one is somewhat unnecessary to do because the Logic unit consists of two 4-bit numbers being AND'ed together. There is a single AND gate for each pair of A and B. The result of the operation will only be true if both A and B are high.

Boolean Expression

$$F = AB$$

BCD Decoder

Truth Table

A	B	C	D	a	b	c	d	e	f	g	#
0	0	0	0	1	1	1	1	1	1	0	0
0	0	0	1	0	1	1	0	0	0	0	1
0	0	1	0	1	1	0	1	1	0	1	2
0	0	1	1	1	1	1	1	0	0	1	3
0	1	0	0	0	1	1	0	0	1	1	4
0	1	0	1	1	0	1	1	0	1	1	5
0	1	1	0	1	0	1	1	1	1	1	6
0	1	1	1	1	1	1	0	0	0	0	7
1	0	0	0	1	1	1	1	1	1	1	8
1	0	0	1	1	1	1	1	0	1	1	9

Karnaugh Map

Explanation

Each output of the BCD Decoder Requires it's own K-map and Boolean Expression. The K-maps for each letter a-g (output) Represent their value for each number that would be displayed on the Seven segment display. For instance the input 'a' will be low only for the values 1 and 4 (see below).



output: a

AB \ CD	00	01	11	10
00	1	0	0	1
01	0	1	0	1
11	1	1	0	0
10	1	1	0	0

output: b

AB \ CD	00	01	11	10
00	1	1	1	1
01	1	0	1	1
11	1	1	1	1
10	1	0	1	1

output: c

AB \ CD	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	0	1	1	1

output: d

AB \ CD	00	01	11	10
00	1	0	0	1
01	0	1	0	0
11	1	1	0	0
10	1	1	0	1

output: e

AB \ CD	00	01	11	10
00	1	0	0	1
01	0	0	0	0
11	0	0	0	0
10	1	1	0	0

output: f

AB \ CD	00	01	11	10
00	1	1	0	1
01	0	1	0	0
11	0	0	0	0
10	0	1	0	1

output: g

AB \ CD	00	01	11	10
00	0	1	1	1
01	0	1	1	1
11	1	0	1	1
10	1	1	1	1

Boolean Expression:

$$a = (A' \& B' \& C' \& D') \vee (A' \& B' \& C \& D') \vee (A' \& B \& C' \& D') \vee (A \& B' \& C' \& D') \vee (A \& B \& C \& D)$$

$$b = (A' \& B' \& C' \& D') \vee (A' \& B \& C \& D') \vee (A \& B \& C' \& D') \vee (A \& B' \& C' \& D) \vee (A \& B \& C \& D)$$

$$c = (A' \& B' \& C' \& D') \vee (A' \& B \& C' \& D') \vee (A' \& B \& C \& D') \vee (A \& B' \& C \& D) \vee (A \& B \& C \& D)$$

$$d = (A' \& B' \& C' \& D') \vee (A' \& B' \& C \& D') \vee (A \& B' \& C \& D') \vee (A \& B \& C' \& D) \vee (A \& B \& C \& D)$$

$$e = (A' \& B' \& C' \& D') \vee (A' \& B \& C' \& D') \vee (A' \& B \& C \& D') \vee (A \& B \& C' \& D') \vee (A \& B \& C \& D)$$

$$f = (A' \& B' \& C' \& D') \vee (A' \& B' \& C' \& D) \vee (A' \& B \& C \& D') \vee (A \& B \& C' \& D') \vee (A \& B \& C \& D)$$

$$g = (A' \& B' \& C' \& D) \vee (A' \& B \& C' \& D) \vee (A \& B' \& C' \& D) \vee (A \& B \& C' \& D) \vee (A \& B \& C \& D)$$

NOTE: Above expression and truth table were built using the provided BCD Seven Segment Decoder (SWE-350) and the reference (GeeksforGeeks, 2019).

PoormansALU

Truth Table

Mux Out	Arith Op													
sel1	sel0	a3	a2	a1	a0	b3	b2	b1	b0	f3	f2	f1	f0	cout
sel1 = '1' Output = Result from Boolean Logic Unit														
1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	1	0	0	0	1	0
1	0	0	0	1	1	0	0	0	1	0	0	0	0	0
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0
1	0	0	1	0	1	0	1	1	1	0	1	0	1	0
1	0	0	1	1	1	0	1	1	1	0	1	1	1	0
sel1 = '0' Output = Result from Arithmetic Unit, sel0 = '0' (Addition)														
0	1	1	0	0	0	1	0	0	0	0	0	0	0	1
0	1	0	1	0	0	0	1	0	0	1	0	0	0	1
0	1	0	1	1	1	0	1	1	1	1	1	1	0	1
0	1	1	1	0	1	1	1	0	1	1	0	1	0	1
0	1	0	0	0	1	0	0	1	0	0	0	1	1	0
sel1 = '0' Output = Result from Arithmetic Unit, sel0 = '1' (Subtraction)														
0	1	1	0	0	0	0	1	1	0	0	0	1	0	1
0	1	0	1	0	0	0	0	1	0	0	0	1	0	1
0	1	1	1	1	1	1	1	1	1	0	0	0	0	1
0	1	1	1	0	1	1	0	0	1	0	1	0	0	1
0	1	0	0	0	1	0	0	0	1	0	0	0	0	1



Karnaugh Map & Boolean Expression

I omitted this K-map and boolean expression. The basis for each possible result (addition, subtraction, AND), are explained in the K-maps for each individual component circuit's K-map above. As such I did not think it was necessary to write a K-map or boolean expression for this circuit as the desired results are described in each of the above truth tables and k-maps.

PoormansALU_Project

Truth Table

Mux Out	Arith Op																							
sel1	sel0	a 3	a 2	a 1	a 0	b 3	b 2	b 1	b 0	f 6	f 5	f 4	f 3	f 2	f 1	f 0	d 6	d 5	d 4	d 3	d 2	d 1	d 0	count
sel1 = '1' Output = Result from Boolean Logic Unit																								
1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	0	0	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1	1	0	1
1	0	0	0	1	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1	1	0	1
1	0	0	0	1	1	0	0	1	1	0	0	0	0	0	0	0	1	0	0	1	1	1	1	1
1	0	0	1	0	1	0	1	1	1	0	0	0	0	0	0	0	0	0	1	0	0	1	0	1
1	0	1	1	1	1	1	1	1	1	0	0	0	0	1	1	0	0	0	1	0	0	1	0	1
sel1 = '0' Output = Result from Arithmetic Unit, sel0 = '0' (Addition)																								
0	1	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	1
0	1	0	1	0	0	0	1	0	0	0	0	0	0	1	1	0	0	1	0	0	1	0	0	0
0	1	0	1	1	1	0	1	1	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0	1
0	1	1	1	0	1	1	1	0	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0	1
0	1	0	0	0	1	0	0	1	0	0	0	0	0	0	0	0	0	1	1	0	0	0	0	0
sel1 = '0' Output = Result from Arithmetic Unit, sel0 = '1' (Subtraction)																								
0	1	1	0	0	0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	1
0	1	0	1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	1	1	0	0	1	1
0	1	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0	1
0	1	1	1	0	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1
0	1	0	0	0	1	0	0	0	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0	1



Karnaugh Map & Boolean Expression

I omitted this K-map and boolean expression. The basis for each possible result (addition, subtraction, AND), are explained in the K-maps for each individual component circuit's K-map above. As such I did not think it was necessary to write a K-map or boolean expression for this circuit as the desired results are described in each of the above truth tables and k-maps.

VLSI Design

4-bit Adder Subtractor (Arithmetic Unit)

Arithmetic Unit VHDL Code Screenshots

Dataflow

```
LIBRARY ieee;
USE ieee.std_logic_1164.all ;

ENTITY four_bit_adder_subtractor IS
PORT(
    cin      : IN STD_LOGIC;
    a        : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
    b        : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
    cout     : OUT STD_LOGIC;
    sum      : OUT STD_LOGIC_VECTOR(3 DOWNTO 0)
);
END four_bit_adder_subtractor;

ARCHITECTURE dataflow OF four_bit_adder_subtractor IS
    SIGNAL i1, i2, i3 : STD_LOGIC;
BEGIN
    sum(0) <= (cin XOR (a(0) XOR (b(0) XOR cin)));
    i1     <= (a(0) AND (b(0) XOR cin)) OR (cin AND (a(0) XOR (b(0) XOR cin)));

    sum(1) <= (i1 XOR (a(1) XOR (b(1) XOR cin)));
    i2     <= (a(1) AND (b(1) XOR cin)) OR (i1 AND (a(1) XOR (b(1) XOR cin)));

    sum(2) <= (i2 XOR (a(2) XOR (b(2) XOR cin)));
    i3     <= (a(2) AND (b(2) XOR cin)) OR (i2 AND (a(2) XOR (b(2) XOR cin)));

    sum(3) <= (i3 XOR (a(3) XOR (b(3) XOR cin)));
    cout  <= (a(3) AND (b(3) XOR cin)) OR (i3 AND (a(3) XOR (b(3) XOR cin)));

END dataflow;
```

Structural

```
LIBRARY ieee;
USE ieee.std_logic_1164.all ;

ENTITY four_bit_adder_subtractor IS
PORT(
    cin      : IN STD_LOGIC;
    a        : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
    b        : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
    cout     : OUT STD_LOGIC;
    sum      : OUT STD_LOGIC_VECTOR(3 DOWNTO 0)
);
END four_bit_adder_subtractor;

ARCHITECTURE structural OF four_bit_adder_subtractor IS
    COMPONENT full_adder IS
        PORT(
            x : IN STD_LOGIC;
            y : IN STD_LOGIC;
            cin : IN STD_LOGIC;
            sum : OUT STD_LOGIC;
            cout: OUT STD_LOGIC
        );
    END COMPONENT;

    SIGNAL c1, c2, c3, c4 : STD_LOGIC;


    BEGIN
        fa0: full_adder(a(0), (b(0) XOR cin), cin, sum(0), c1);
        fa1: full_adder(a(1), (b(1) XOR cin), c1, sum(1), c2);
        fa2: full_adder(a(2), (b(2) XOR cin), c2, sum(2), c3);
        fa3: full_adder(a(3), (b(3) XOR cin), c3, sum(3), cout);
    END structural;
```

Arithmetic Unit Simulations

(add: cin = 0 a+b, sub: cin = 1 a-b) a = 1110, b = 1010



a=0011, b = 0010

 

Quad 2:1 Multiplexer

Quad 2:1 MUX VHDL Code Screenshots

Behavioral Model

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY quad_2_1_mux IS
    PORT (
        enb : IN STD_LOGIC;
        sel  : IN STD_LOGIC;
        a    : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        b    : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        f    : OUT STD_LOGIC_VECTOR(3 DOWNTO 0)
    );
END quad_2_1_mux;

ARCHITECTURE behavioral OF quad_2_1_mux IS
BEGIN
    PROCESS(enb, sel, a, b)
    BEGIN
        IF (enb = '1') THEN
            f <= "0000";
        ELSIF (sel = '1') THEN
            f <= b;
        ELSIF (sel = '0') THEN
            f <= a;
        ELSE
            f <= "0000";
        END IF;
    END PROCESS;
END behavioral;
```

Dataflow Model

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY quad_2_1_mux IS
    PORT (
        enb : IN STD_LOGIC;
        sel  : IN STD_LOGIC;
        a    : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        b    : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        f    : OUT STD_LOGIC_VECTOR(3 DOWNTO 0)
    );
END quad_2_1_mux;

ARCHITECTURE data_flow OF quad_2_1_mux IS
BEGIN
    f(0) <= (a(0) AND NOT enb AND NOT sel) OR (b(0) AND NOT enb AND sel);
    f(1) <= (a(1) AND NOT enb AND NOT sel) OR (b(1) AND NOT enb AND sel);
    f(2) <= (a(2) AND NOT enb AND NOT sel) OR (b(2) AND NOT enb AND sel);
    f(3) <= (a(3) AND NOT enb AND NOT sel) OR (b(3) AND NOT enb AND sel);
END data_flow;
```

Structural

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY quad_2_1_mux IS
    PORT (
        E : IN STD_LOGIC;
        S : IN STD_LOGIC;
        A : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        B : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        F : OUT STD_LOGIC_VECTOR(3 DOWNTO 0)
    );
END quad_2_1_mux;

ARCHITECTURE structural OF quad_2_1_mux IS
    COMPONENT e2_1_mux IS
        PORT (
            enb: IN STD_LOGIC;
            sel: IN STD_LOGIC;
            a : IN STD_LOGIC;
            b : IN STD_LOGIC;
            f : OUT STD_LOGIC
        );
    END COMPONENT;

    BEGIN

        emux0 : e2_1_mux PORT MAP(E, S, A(0), B(0), F(0));
        emux1 : e2_1_mux PORT MAP(E, S, A(1), B(1), F(1));
        emux2 : e2_1_mux PORT MAP(E, S, A(2), B(2), F(2));
        emux3 : e2_1_mux PORT MAP(E, S, A(3), B(3), F(3));

    END structural;

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;


ENTITY e2_1_mux IS
    PORT (
        enb: IN STD_LOGIC;
        sel: IN STD_LOGIC;
        a : IN STD_LOGIC;
        b : IN STD_LOGIC;
        f : OUT STD_LOGIC
    );
END e2_1_mux;

ARCHITECTURE data_flow OF e2_1_mux IS
    BEGIN
        f <= (NOT enb AND ((a AND NOT sel) OR (b AND sel)));
    END data_flow;


```

Quad 2:1 MUX Simulations:

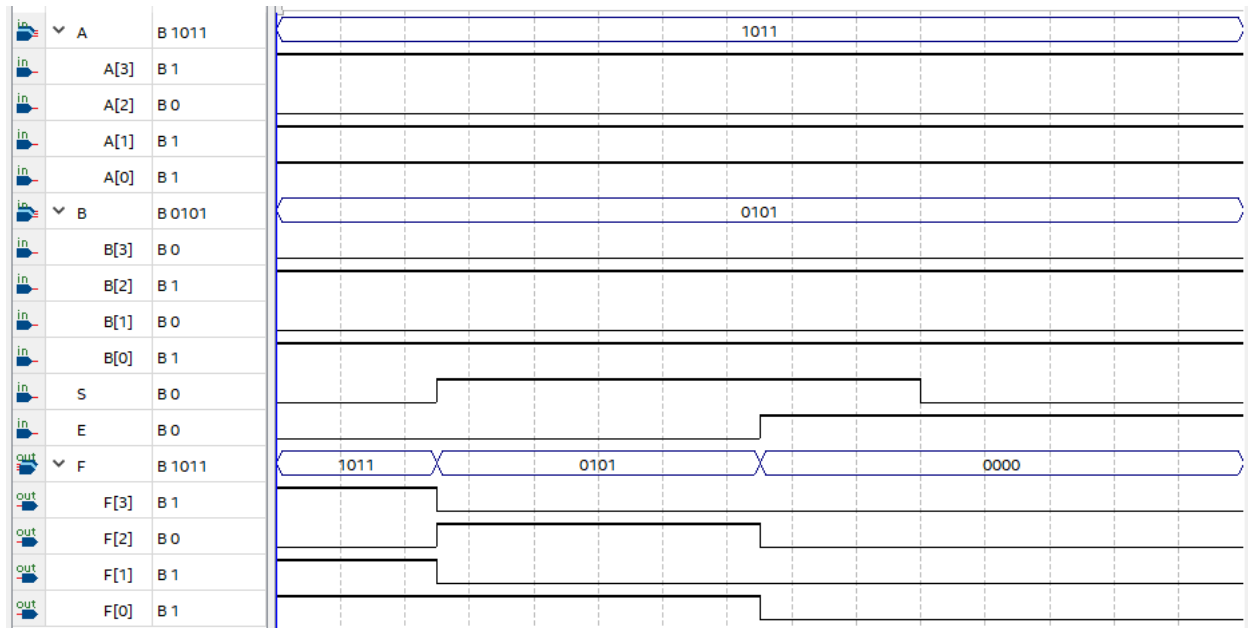a = 1011 b = 0101 (output = b if sel(0) = 0) **Note:** a(0) & b(0) are LSB



a = 1001 b = 1101

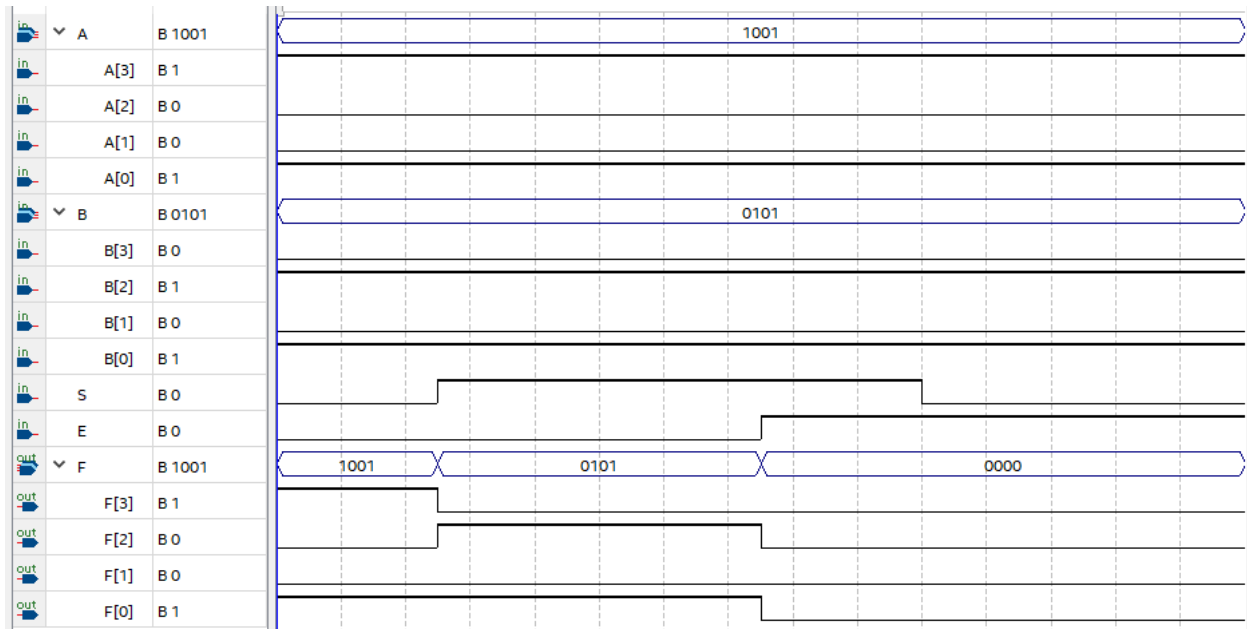

IP Core Code Screenshot

```

LIBRARY lpm;
USE lpm.lpm_components.all;

ENTITY ip_core_quad_mux IS
    PORT
    (
        data0x      : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        data1x      : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        sel         : IN STD_LOGIC;
        result       : OUT STD_LOGIC_VECTOR (3 DOWNTO 0)
    );
END ip_core_quad_mux;

ARCHITECTURE SYN OF ip_core_quad_mux IS
    -- type STD_LOGIC_2D is array (NATURAL RANGE <>, NATURAL RANGE <>) of STD_LOGIC;

    SIGNAL sub_wire0 : STD_LOGIC_VECTOR (3 DOWNTO 0);
    SIGNAL sub_wire1 : STD_LOGIC_2D (1 DOWNTO 0, 3 DOWNTO 0);
    SIGNAL sub_wire2 : STD_LOGIC_VECTOR (3 DOWNTO 0);
    SIGNAL sub_wire3 : STD_LOGIC;
    SIGNAL sub_wire4 : STD_LOGIC_VECTOR (0 DOWNTO 0);
    SIGNAL sub_wire5 : STD_LOGIC_VECTOR (3 DOWNTO 0);

BEGIN
    sub_wire2 <= data0x(3 DOWNTO 0);
    sub_wire0 <= data1x(3 DOWNTO 0);
    sub_wire1(1, 0) <= sub_wire0(0);
    sub_wire1(1, 1) <= sub_wire0(1);
    sub_wire1(1, 2) <= sub_wire0(2);
    sub_wire1(1, 3) <= sub_wire0(3);
    sub_wire1(0, 0) <= sub_wire2(0);
    sub_wire1(0, 1) <= sub_wire2(1);
    sub_wire1(0, 2) <= sub_wire2(2);
    sub_wire1(0, 3) <= sub_wire2(3);
    sub_wire3 <= sel;
    sub_wire4(0) <= sub_wire3;
    result <= sub_wire5(3 DOWNTO 0);

    LPM_MUX_component : LPM_MUX
    GENERIC MAP (
        lpm_size => 2,
        lpm_type => "LPM_MUX",
        lpm_width => 4,
        lpm_widths => 1
    )
    PORT MAP (
        data => sub_wire1,
        sel => sub_wire4,
        result => sub_wire5
    );

```

Boolean Logic Unit

Boolean Logic Unit VHDL Code Screenshots

Dataflow

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY palu_bool_logic_unit IS
    PORT(
        a : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        b : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        f : OUT STD_LOGIC_VECTOR(3 DOWNTO 0)
    );
END palu_bool_logic_unit;

ARCHITECTURE dataflow OF palu_bool_logic_unit IS
    BEGIN
        f <= a AND b;
    END dataflow;
```

Behavioral

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY palu_bool_logic_unit IS
    PORT(
        a : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        b : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        f : OUT STD_LOGIC_VECTOR(3 DOWNTO 0)
    );
END palu_bool_logic_unit;

ARCHITECTURE behavioral OF palu_bool_logic_unit IS
    BEGIN
        PROCESS(a, b)
        BEGIN
            IF (a = "1111" AND b = "1111") THEN
                f <= "1111";
            ELSE
                f <= "0000";
            END IF;
        END PROCESS;
    END behavioral;
```


Structural

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY palu_bool_logic_unit IS
    PORT(
        A : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        B : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        F : OUT STD_LOGIC_VECTOR(3 DOWNTO 0)
    );
END palu_bool_logic_unit;

ARCHITECTURE structural OF palu_bool_logic_unit IS
    COMPONENT and_bool_unit IS
        PORT(
            a : IN STD_LOGIC;
            b : IN STD_LOGIC;
            f : OUT STD_LOGIC
        );
    END COMPONENT;
    BEGIN
        abu0 : and_bool_unit PORT MAP(A(0), B(0), F(0));
        abu1 : and_bool_unit PORT MAP(A(1), B(1), F(1));
        abu2 : and_bool_unit PORT MAP(A(2), B(2), F(2));
        abu3 : and_bool_unit PORT MAP(A(3), B(3), F(3));
    END structural;

```

```



LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY and_bool_unit IS
    PORT(
        a : IN STD_LOGIC;
        b : IN STD_LOGIC;
        f : OUT STD_LOGIC
    );
END and_bool_unit;

ARCHITECTURE structural OF and_bool_unit IS
    BEGIN
        f <= a AND b;
    END structural;

```

Boolean Logic Unit Simulations

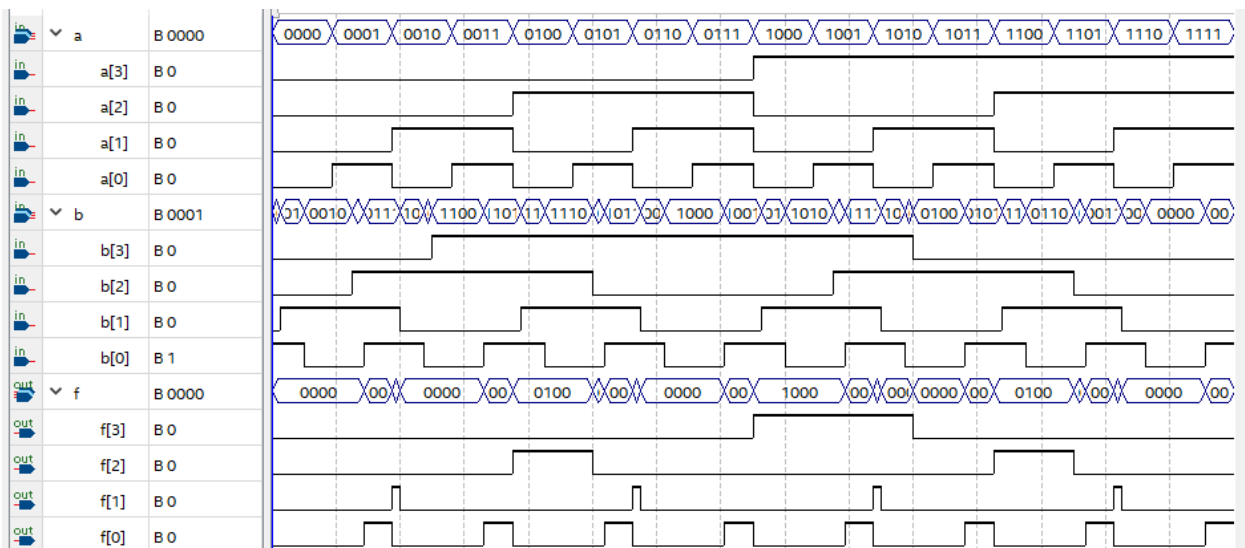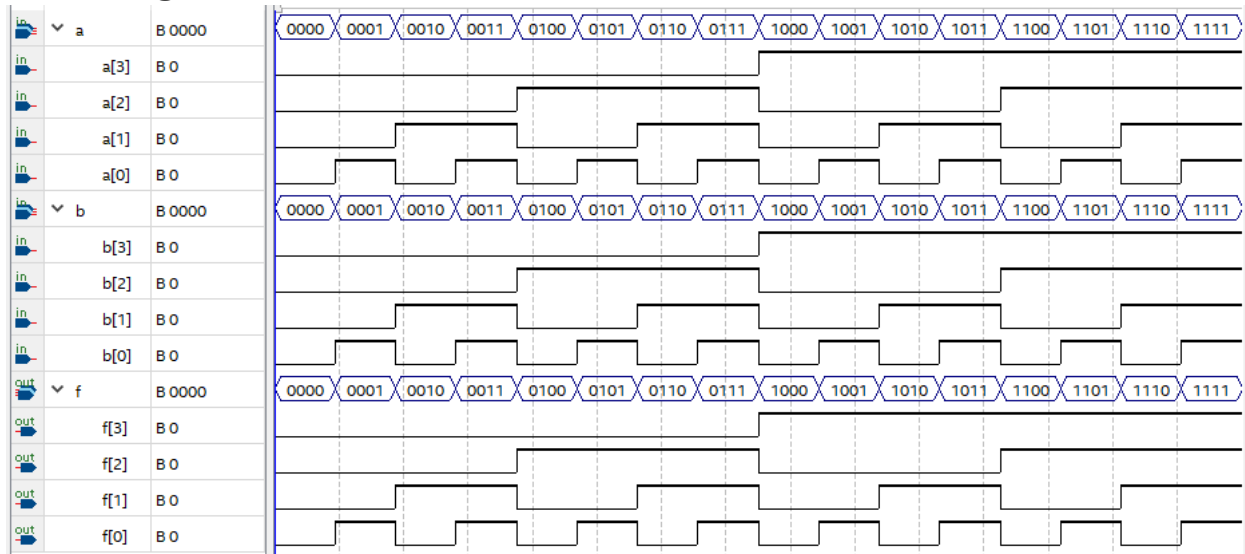

BCD Decoder

BCD Decoder VHDL Code Screenshot (Code from SWE-350)

```


LIBRARY ieee;
USE ieee.std_logic_1164.all ;

ENTITY bcd_7segment IS
    PORT(bcd_in : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
         seven_segment_out : OUT STD_LOGIC_VECTOR (6 DOWNTO 0));
END bcd_7segment ;

ARCHITECTURE Behavioral OF bcd_7segment IS
BEGIN
    PROCESS(bcd_in)
    BEGIN
        CASE bcd_in IS
            WHEN "0000" =>
                seven_segment_out <= not "0111111" ;
            WHEN "0001" =>
                seven_segment_out <= not "0000110" ;
            WHEN "0010" =>
                seven_segment_out <= not "1011011" ;
            WHEN "0011" =>
                seven_segment_out <= not "1001111" ;
            WHEN "0100" =>
                seven_segment_out <= not "1100110" ;
            WHEN "0101" =>
                seven_segment_out <= not "1101101" ;
            WHEN "0110" =>
                seven_segment_out <= not "1111101" ;
            WHEN "0111" =>
                seven_segment_out <= not "0000111" ;
            WHEN "1000" =>
                seven_segment_out <= not "1111111" ;
            WHEN "1001" =>
                seven_segment_out <= not "1100111" ;
            WHEN OTHERS =>
                seven_segment_out <= not "1111111" ;
        END CASE;
    END PROCESS;
END Behavioral;

```

BCD Decoder Simulation

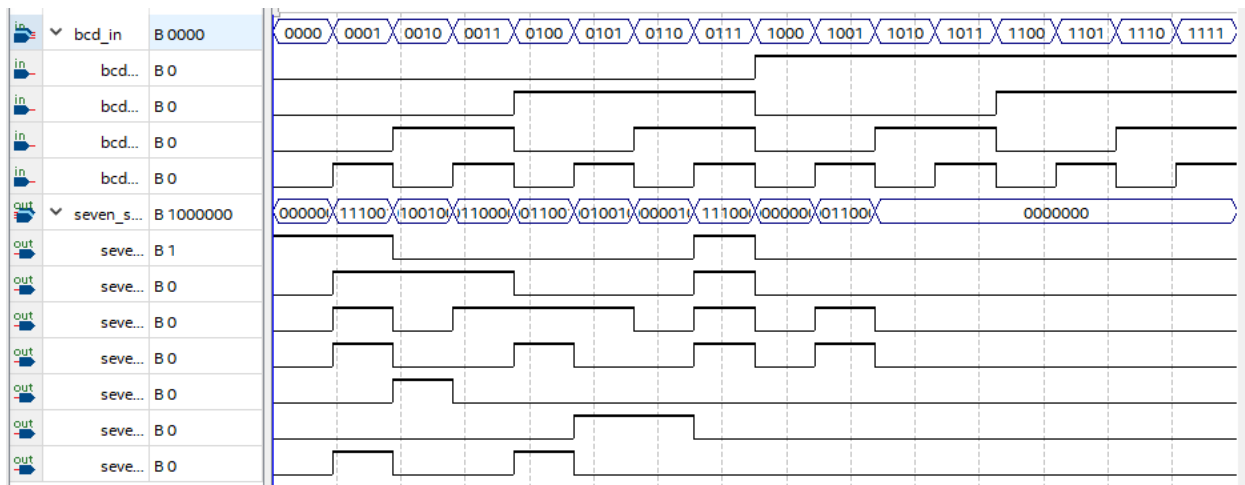

BCD Decoder(extended) VHDL Code Screenshot


Note: This code is derived from the code above (from SWE350) but includes some additions to handle numbers that are 4-bits wide with two seven segment displays

```
LIBRARY ieee;
USE ieee.std_logic_1164.all ;

ENTITY bcd_7segment IS
  PORT(
    bcd_in : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    seven_segment_out : OUT STD_LOGIC_VECTOR (6 DOWNTO 0);
    seven_segment_out1 : OUT STD_LOGIC_VECTOR (6 DOWNTO 0)
  );
END bcd_7segment ;

ARCHITECTURE Behavioral OF bcd_7segment IS
  BEGIN
    PROCESS(bcd_in)
      BEGIN
        CASE bcd_in IS
          WHEN "0000" => -- x0
            seven_segment_out <= not "0111111" ;
            seven_segment_out1 <= not "0000000" ;
          WHEN "0001" => --x1
            seven_segment_out <= not "0000110" ;
            seven_segment_out1 <= not "0000000" ;
          WHEN "0010" => --x2
            seven_segment_out <= not "1011011" ;
            seven_segment_out1 <= not "0000000" ;
          WHEN "0011" => --x3
            seven_segment_out <= not "1001111" ;
            seven_segment_out1 <= not "0000000" ;
          WHEN "0100" => --x4
            seven_segment_out <= not "1100110" ;
            seven_segment_out1 <= not "0000000" ;
          WHEN "0101" => --x5
            seven_segment_out <= not "1101101" ;
            seven_segment_out1 <= not "0000000" ;
          WHEN "0110" => --x6
            seven_segment_out <= not "1111101" ;
            seven_segment_out1 <= not "0000000" ;
          WHEN "0111" => --x7
            seven_segment_out <= not "0000111" ;
            seven_segment_out1 <= not "0000000" ;
          WHEN "1000" => --x8
            seven_segment_out <= not "1111111" ;
            seven_segment_out1 <= not "0000000" ;
          WHEN "1001" => --x9
            seven_segment_out <= not "1100111" ;
            seven_segment_out1 <= not "0000000" ;
          WHEN "1010" => -- 10
            seven_segment_out <= not "0111111" ;
            seven_segment_out1 <= not "0000110" ;
          WHEN "1011" => --11
            seven_segment_out <= not "0000110" ;
            seven_segment_out1 <= not "0000110" ;
          WHEN "1100" => --12
            seven_segment_out <= not "1011011" ;
            seven_segment_out1 <= not "0000110" ;
          WHEN "1101" => --13
            seven_segment_out <= not "1001111" ;
            seven_segment_out1 <= not "0000110" ;
          WHEN "1110" => --14
            seven_segment_out <= not "1100110" ;
            seven_segment_out1 <= not "0000110" ;
          WHEN "1111" => --15
            seven_segment_out <= not "1101101" ;
            seven_segment_out1 <= not "0000110" ;
          WHEN OTHERS =>
            seven_segment_out <= not "1111111" ;
            seven_segment_out1 <= not "1111111" ;
        END CASE;
      END PROCESS;
    END Behavioral;
```

(extended) BCD Decoder Simulation

 

PoormansALU VHDL Code Screenshot

```

ENTITY poormansALU IS
    PORT(
        operand_one : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        operand_two : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        selector     : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
        result_out   : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
        carry_out    : OUT STD_LOGIC
    );
END poormansALU;

ARCHITECTURE dataflow OF poormansALU IS
    COMPONENT four_bit_adder_subtractor IS
        PORT(
            cin      : IN STD_LOGIC;
            a        : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
            b        : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
            cout     : OUT STD_LOGIC;
            sum      : OUT STD_LOGIC_VECTOR(3 DOWNTO 0)
        );
    END COMPONENT;

    COMPONENT palu_bool_logic_unit IS
        PORT(
            u : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
            w : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
            e : OUT STD_LOGIC_VECTOR(3 DOWNTO 0)
        );
    END COMPONENT;

    COMPONENT quad_2_1_mux IS
        PORT(
            enb : IN STD_LOGIC;
            sel : IN STD_LOGIC;
            x   : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
            y   : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
            f   : OUT STD_LOGIC_VECTOR(3 DOWNTO 0)
        );
    END COMPONENT;


    SIGNAL mid1, mid12 : STD_LOGIC_VECTOR(3 DOWNTO 0);

    BEGIN
        fas1 : four_bit_adder_subtractor PORT MAP(selector(0), operand_one, operand_two, carry_out, mid1);
        pblu : palu_bool_logic_unit PORT MAP(operand_one, operand_two, mid12);
        qdmx : quad_2_1_mux PORT MAP('0', selector(1), mid1, mid12, result_out);
    END dataflow;


```



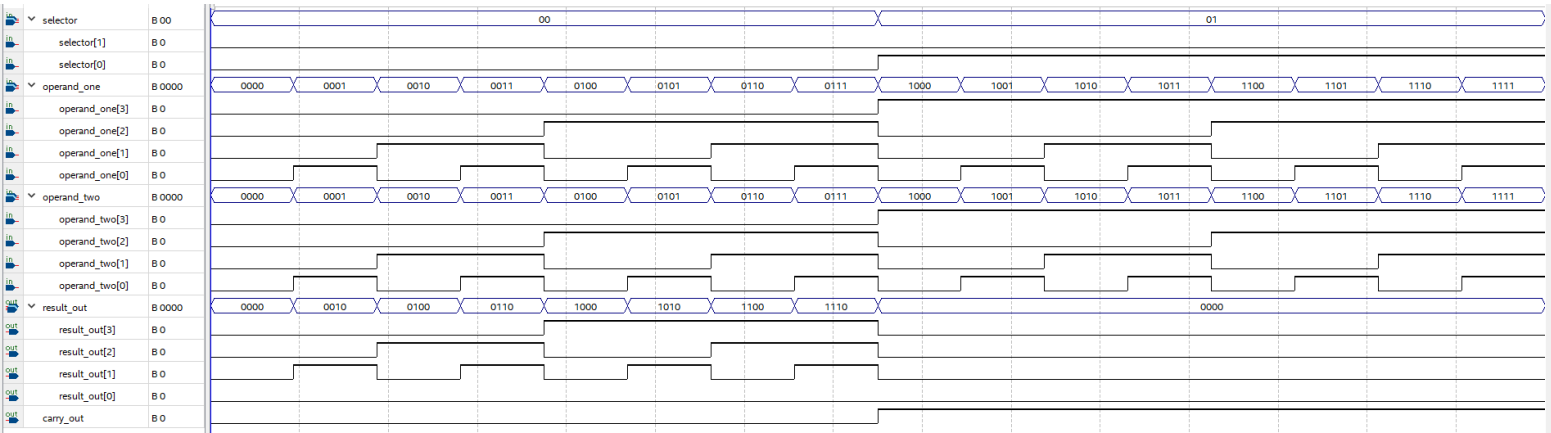PoormansALU Waveform Simulation (addition & subtraction)



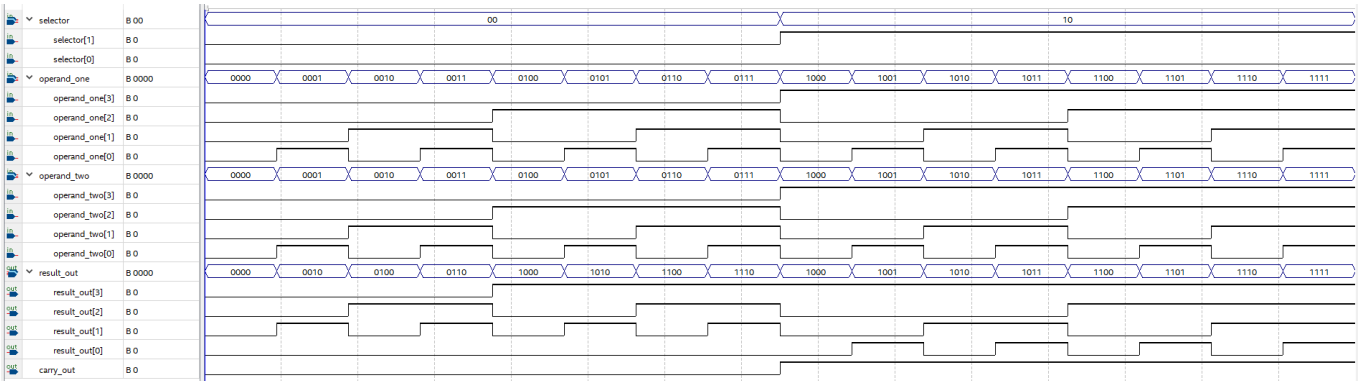PoormansALU Waveform Simulation (boolean logic & addition)



PoormansALU Project VHDL Code Screenshot

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY PoormansALU_Project IS
    PORT(
        operand_A      : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        operand_b      : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        select_sw      : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
        disp_output     : OUT STD_LOGIC_VECTOR(6 DOWNTO 0);
        disp_output2    : OUT STD_LOGIC_VECTOR(6 DOWNTO 0);
        carry_output    : OUT STD_LOGIC
    );
END PoormansALU_Project;

ARCHITECTURE structural OF PoormansALU_Project IS

    COMPONENT poormansALU IS
        PORT(
            operand_one : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
            operand_two : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
            selector     : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
            result_out   : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
            carry_out    : OUT STD_LOGIC
        );
    END COMPONENT;


    COMPONENT bcd_7segment IS
        PORT(
            bcd_in : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
            seven_segment_out : OUT STD_LOGIC_VECTOR (6 DOWNTO 0);
            seven_segment_out1 : OUT STD_LOGIC_VECTOR (6 DOWNTO 0)
        );
    END COMPONENT;

    SIGNAL s1, s2 : STD_LOGIC_VECTOR(3 DOWNTO 0);


    BEGIN
        palu : poormansALU PORT MAP(operand_A, operand_B, select_sw, s1, carry_output);
        bcdc : bcd_7segment PORT MAP(s1, disp_output, disp_output2);
END structural;

```

 PoormansALU Project Waveform Simulation (addition & subtraction)



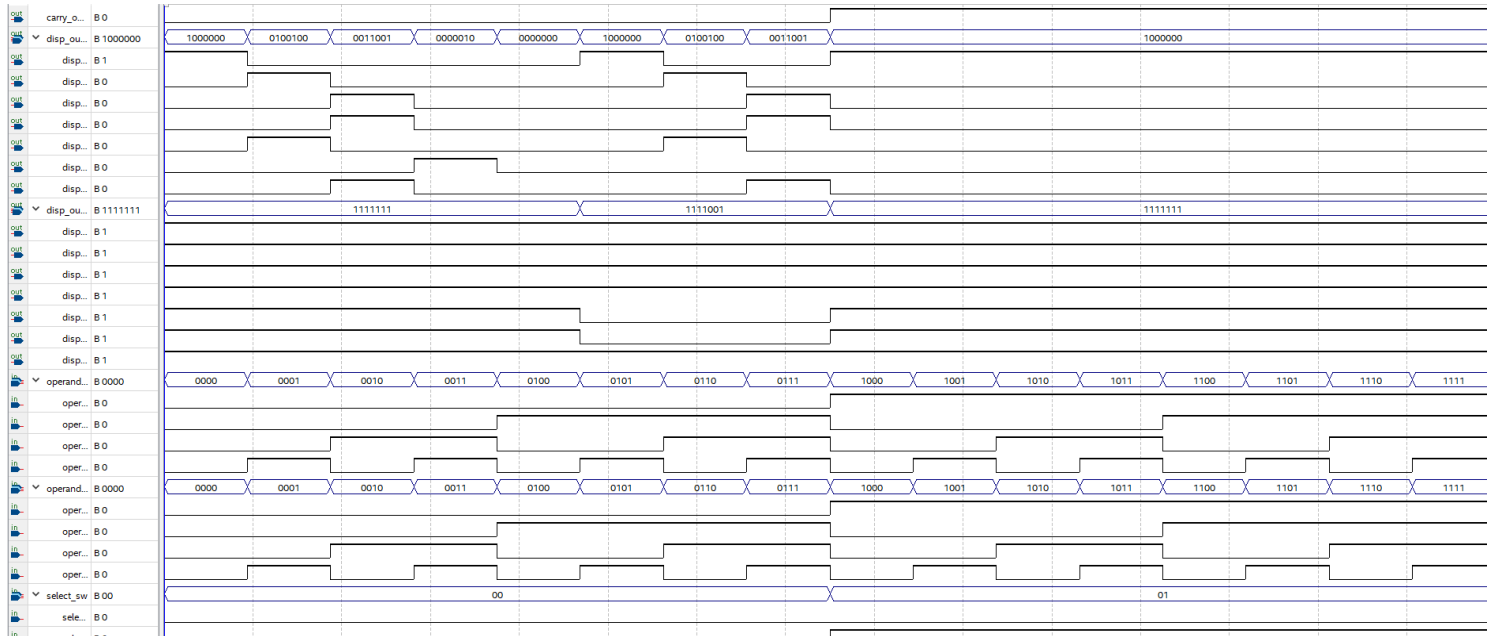PoormansALU Project Waveform Simulation (boolean logic & addition)



Risks & Issues

N/A. - this is the final release for this project.

Other Documentation

PoormansALU - Verilog

```
module poormansALU(
    input    [3:0] operand_one,
    input    [3:0] operand_two,
    input    [1:0] selector,
    output   [3:0] result_out,
    output   [3:0] carry_out
);

    wire mid11, mid12;

    four_bit_adder_subtractor fbas(selector[0], operand_one, operand_two, carry_out, mid11);
    palu_bool_logic_unit      pblu(operand_one, operand_two, mid12);
    quad_2_1_mux              qdmx(0, selector[1], mid11, mid12, result_out);

endmodule
```

PoormansALU_Project - Verilog

```
module poormansALU(
    input    [3:0] operand_A,
    input    [3:0] operand_B,
    input    [1:0] selector_sw,
    output   [3:0] disp_output,
    output   [3:0] disp_output2,
    output   [3:0] carry_output
);

    wire [3:0] mid11, [3:0] mid12, mid13;

    poormansALU palu(operand_A, operand_B, select_sw, mid13, carry_output);
    bcd_7segment bcdc(mid13, disp_output, disp_output2);

endmodule
```


Extended BCD Decoder - Verilog

```
module bcd_7segment(  
    input [3:0] bcd,  
    output reg [6:0] seven_segment,  
    output reg [6:0] seven_segment2  
);  
  
always @ (bcd)  
begin  
    case (bcd)  
        4'b0000 : //x0  
        begin seven_segment = ~ 7'b0111111;  
              seven_segment2 = ~ 7'b1111111;  
        end  
  
        4'b0001 : //x1  
        begin seven_segment = ~ 7'b0000110;  
              seven_segment2 = ~ 7'b1111111;  
        end  
  
        4'b0010 : //x2  
        begin seven_segment = ~ 7'b1011011;  
              seven_segment2 = ~ 7'b1111111;  
        end  
  
        4'b0011 : //x3  
        begin seven_segment = ~ 7'b1001111;  
              seven_segment2 = ~ 7'b1111111;  
        end  
  
        4'b0100 : //x4  
        begin seven_segment = ~ 7'b1100110;  
              seven_segment2 = ~ 7'b1111111;  
        end  
  
        4'b0101 : //x5  
        begin seven_segment = ~ 7'b1101101;  
              seven_segment2 = ~ 7'b1111111;  
        end  
  
        4'b0110 : //x6  
        begin seven_segment = ~ 7'b1111101;  
              seven_segment2 = ~ 7'b1111111;  
        end  
  
        4'b0111 : //x7  
        begin seven_segment = ~ 7'b0000111;  
              seven_segment2 = ~ 7'b1111111;  
        end  
  
        4'b1000 : //x8  
        begin seven_segment = ~ 7'b1111111;  
              seven_segment2 = ~ 7'b1111111;  
        end  
  
        4'b1001 : //x9  
        begin seven_segment = ~ 7'b1111111;  
              seven_segment2 = ~ 7'b1111111;  
        end  
  
        4'b1010 : //10  
        begin seven_segment = ~ 7'b0111111;  
              seven_segment2 = ~ 7'b0000110;  
        end  
  
        4'b1011 : //11  
        begin seven_segment = ~ 7'b0000110;  
              seven_segment2 = ~ 7'b0000110;  
        end  
  
        4'b1100 : //12  
        begin seven_segment = ~ 7'b1011011;  
              seven_segment2 = ~ 7'b0000110;  
        end  
  
        4'b1101 : //13  
        begin seven_segment = ~ 7'b1001111;  
              seven_segment2 = ~ 7'b0000110;  
        end  
  
        4'b1110 : //14  
        begin seven_segment = ~ 7'b1100110;  
              seven_segment2 = ~ 7'b0000110;  
        end  
  
        4'b1111 : //15  
        begin seven_segment = ~ 7'b1110110;  
              seven_segment2 = ~ 7'b0000110;  
        end  
  
        default : begin seven_segment = ~ 7'b1111111;  
                      seven_segment2 = ~ 7'b1111111;  
        end  
    endcase  
end  
endmodule
```

Quad 2:1 MUX - Verilog

```
module quad_2_1_mux(input [3:0] a, input [3:0] b, input enb, sel, output [3:0] f);  
    assign f[0] = (a[0] & !enb & !sel) | (b[0] & !enb & sel);  
    assign f[1] = (a[1] & !enb & !sel) | (b[1] & !enb & sel);  
    assign f[2] = (a[2] & !enb & !sel) | (b[2] & !enb & sel);  
    assign f[3] = (a[3] & !enb & !sel) | (b[3] & !enb & sel);  
endmodule
```

Boolean Logic Unit - Verilog (AND two 4-bit inputs)

```
module palu_bool_logic_unit(input [3:0] a, input [3:0] b, output [3:0] f);  
    assign f = a & b;  
endmodule
```

4-bit Adder/Subtractor (arithmetic unit) - Verilog

```
module four_bit_adder_subtractor  
(  
    input cin,  
    input [3:0] a,  
    input [3:0] b,  
    output cout,  
    output [3:0] sum  
);  
    wire i1, i2, i3;  
    assign sum[0] = (cin ^ (a[0] ^ (b[0] ^ cin)));  
    assign i1 = (a[0] & (b[0] ^ cin)) | (cin & (a[0] ^ (b[0] ^ cin)));  
    assign sum[1] = (i1 ^ (a[1] ^ (b[1] ^ cin)));  
    assign i2 = (a[1] & (b[1] ^ cin)) | (i1 & (a[1] ^ (b[1] ^ cin)));  
    assign sum[2] = (i2 ^ (a[2] ^ (b[2] ^ cin)));  
    assign i3 = (a[2] & (b[2] ^ cin)) | (i2 & (a[2] ^ (b[2] ^ cin)));  
    assign sum[3] = (i3 ^ (a[3] ^ (b[3] ^ cin)));  
    assign cout = (a[3] & (b[3] ^ cin)) | (i3 & (a[3] ^ (b[3] ^ cin)));  
endmodule
```

Arm Assembly

Error Check Function - alu_module

```
void errorCheck(int userVariable, int lowerBound, int upperBound){
    asm(
        "cmp %0, %2\n"           // Compare userVariable and upperBound
        "ble .check_lower\n"     // Jump to .check_lower if userVariable <= upperBound
        "mov %0, #15\n"         // userVariable = 15
        "b .exit_check\n"        // Jump to .exit_check
        ".check_lower:\n"
        "cmp %0, %1\n"           // Compare userVariable and lowerBound
        "bge .exit_check\n"      // Jump to .exit_check if userVariable >= lowerBound
        "mov %0, #0\n"           // userVariable = 0
        ".exit_check:\n"
        : "+r"(userVariable)     // Output: write to and read from userVariable
        : "r"(lowerBound), "r"(upperBound) // Inputs: lowerBound, upperBound
        : "cc"                   // Clobbered registers: condition code flags
    );
}
```

WriteToParallelPort Function - hardware_module

```
unsigned int jpi_address = jpi_port;

asm volatile(
    "ldr r1, [%[jpi_address]] \n" // Load the value at the jpi_address into r1
    "str %[first_operand], [r1] #0\n" // Store the first operand to the lower 4 bits of the data register 1
    "str %[second_operand], [r1] #1\n" // Store the second operand to the upper 4 bits of the data register 1
    :
    : [jpi_address] "r" (&jpi_address), [first_operand] "r" (first_4b_operand), [second_operand] "r" (second_4b_operand)
    : "r1"
);
```

Resources

Documentation – Arm Developer. (n.d.).

<https://developer.arm.com/documentation/dui0473/c/writing-arm-assembly-language>

Writing ARM Assembly (Part 1). (n.d.). Azeria-Labs.

<https://azeria-labs.com/writing-arm-assembly-part-1/>